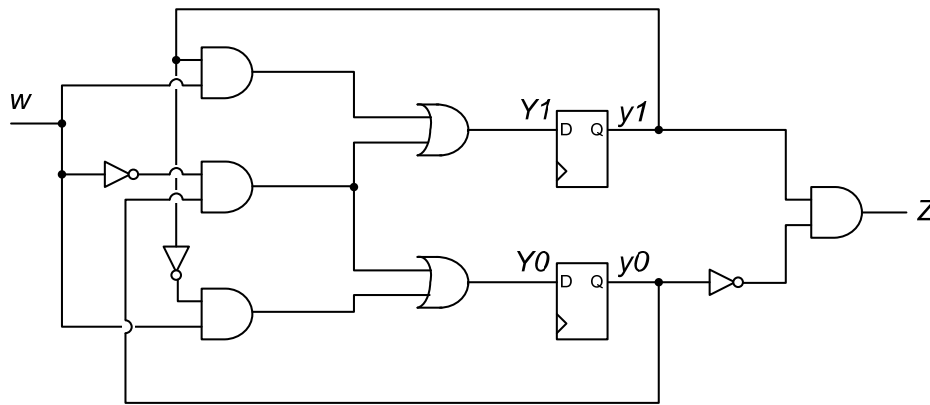


### Practice Assignment 3: Timing

1. Consider the following circuit. The clock connections to the flip-flops are not shown (both flip-flops are clocked by the same clock).




Delay of each logic gate: 1 ns  
Set up time of each flip-flop: 0.2 ns  
Hold time of each flip-flop: 0 ns  
Maximum Clk-to-Q delay of each flip-flop: 0.5 ns  
Minimum Clk-to-Q delay of each flip-flop: 0.1 ns

- What is the maximum frequency of the clock in this circuit (in Mhz) ?
- Suppose the hold time is not 0. What is the largest value for the hold time for which this circuit will still function properly?
- Write a synthesizable VHDL specification of the above circuit using a single process and no "port map"s.

(continued on next page)

2. Consider the following circuit:

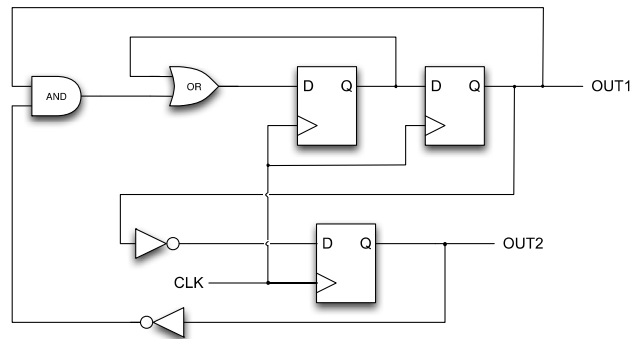

Assume the following:


- Delay of each inverter: 0.6 ns
- Delay of each AND and OR gate: 1 ns
- Set up time of each flip-flop: 0.3 ns
- Hold time of each flip-flop: 0.2 ns
- Maximum Clk-to-Q delay of each flip-flop: 0.5 ns
- Minimum Clk-to-Q delay of each flip-flop: 0 ns

Answer the following questions:

- What is the maximum frequency of this circuit (in Mhz) ?
  - Suppose the minimum Clk-to-Q delay is not 0 ns. What is the smallest value of the minimum Clk-to-Q delay such that there is no hold time violation in this circuit?
3. Suppose a high-end microprocessor is to run at 2Ghz (remember than 2Ghz = 2000 Mhz). Further, suppose the delay of each logic gate is 0.08 ns. Assume the set-up, hold, and Clk-to-Q times of all flip flops are 0. What is the maximum number of gates that can appear in the critical path of this circuit? (note: all the numbers in this question are realistic, and the answer has a huge effect on the logic design of high-end microprocessors... you'll learn more about this in CPEN 411 if you take it).

(continued on next page)

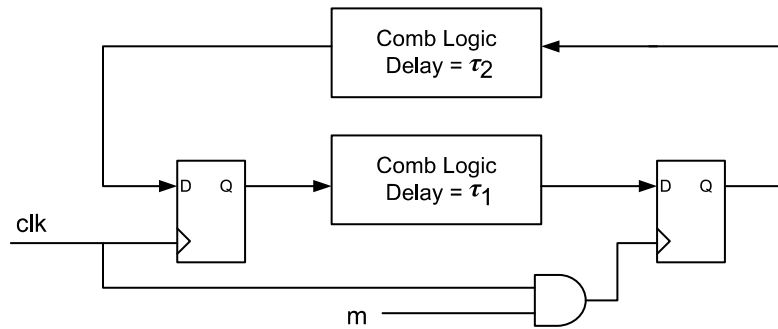4. Consider the following circuit. Note that the second flip-flop's clock input is derived from the clock signal and input signal  $m$  (so the clock only goes high when  $m$  is high).



Assume the following:

Set up time of each flip-flop: 0.3 ns

Hold time of each flip-flop: 0.2 ns

Maximum Clk-to-Q delay of each flip-flop: 0.5 ns

Minimum Clk-to-Q delay of each flip-flop: 0.25 ns

Delay of the AND gate: 1 ns

Suppose we want to run this circuit at 100 Mhz. Answer the following questions:

- What is the *maximum* possible value of  $\tau_1$  that the circuit is guaranteed to work correctly at 100 Mhz? Show your work. If there is no maximum, write  $\infty$ .
- What is the *maximum* possible value of  $\tau_2$  for the circuit to work correctly at 100 Mhz? Show your work. If there is no maximum, write  $\infty$ .
- What is the *minimum* possible value of  $\tau_1$  for the circuit to work correctly at 100 Mhz? Show your work. If there is no minimum, write 0.
- What is the *minimum* possible value of  $\tau_2$  for the circuit to work correctly at 100 Mhz? Show your work. If there is no minimum, write 0.